 



Instruções de Acesso à Memória e de Desvio Condicional

Prof. Alberto F. De Souza
LCAD/DI/UFES
sp1@lcad.inf.ufes.br




lcad
LABORATÓRIO DE COMPUTAÇÃO
DE ALTO DESEMPENHO

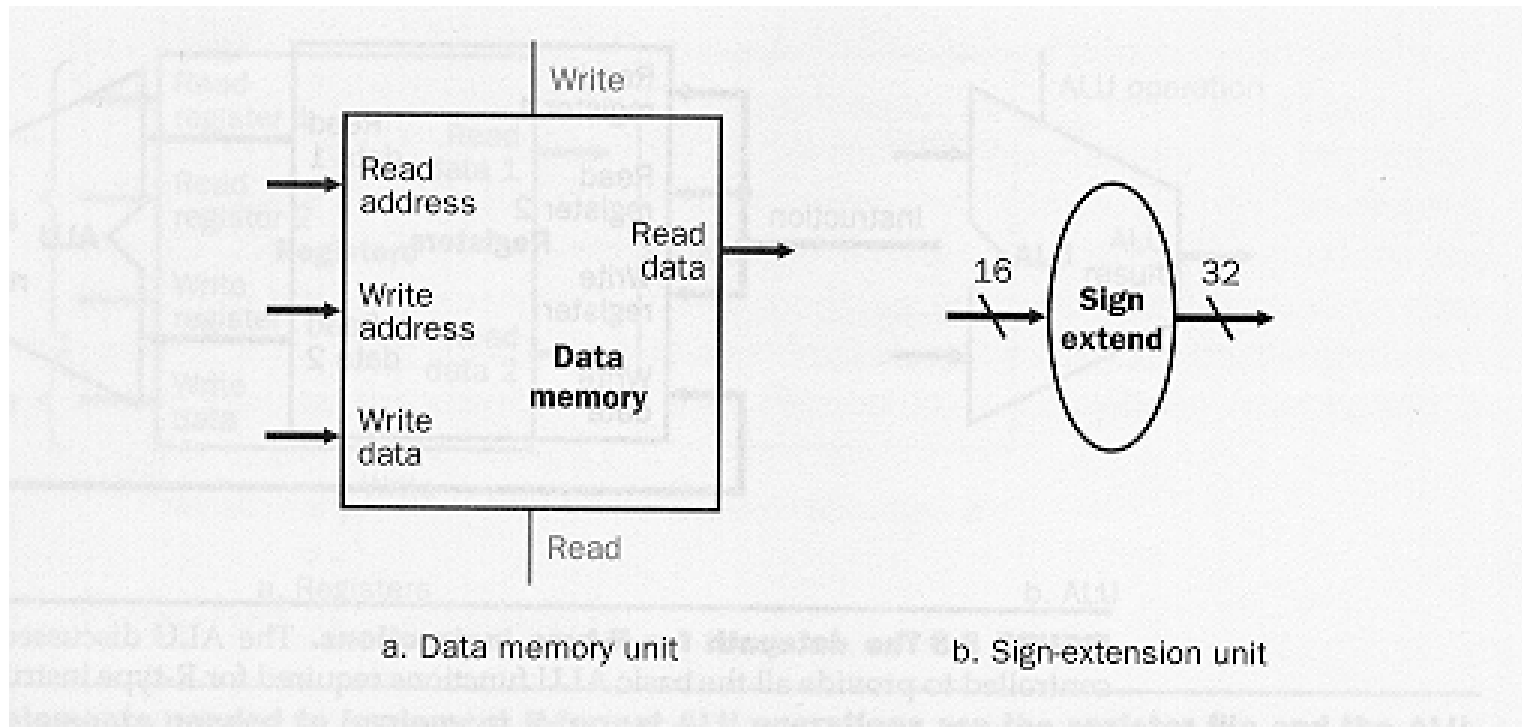- Para implementar as instruções de leitura e escrita na memória, precisamos dos componentes abaixo:






- Eles podem ser organizados como abaixo

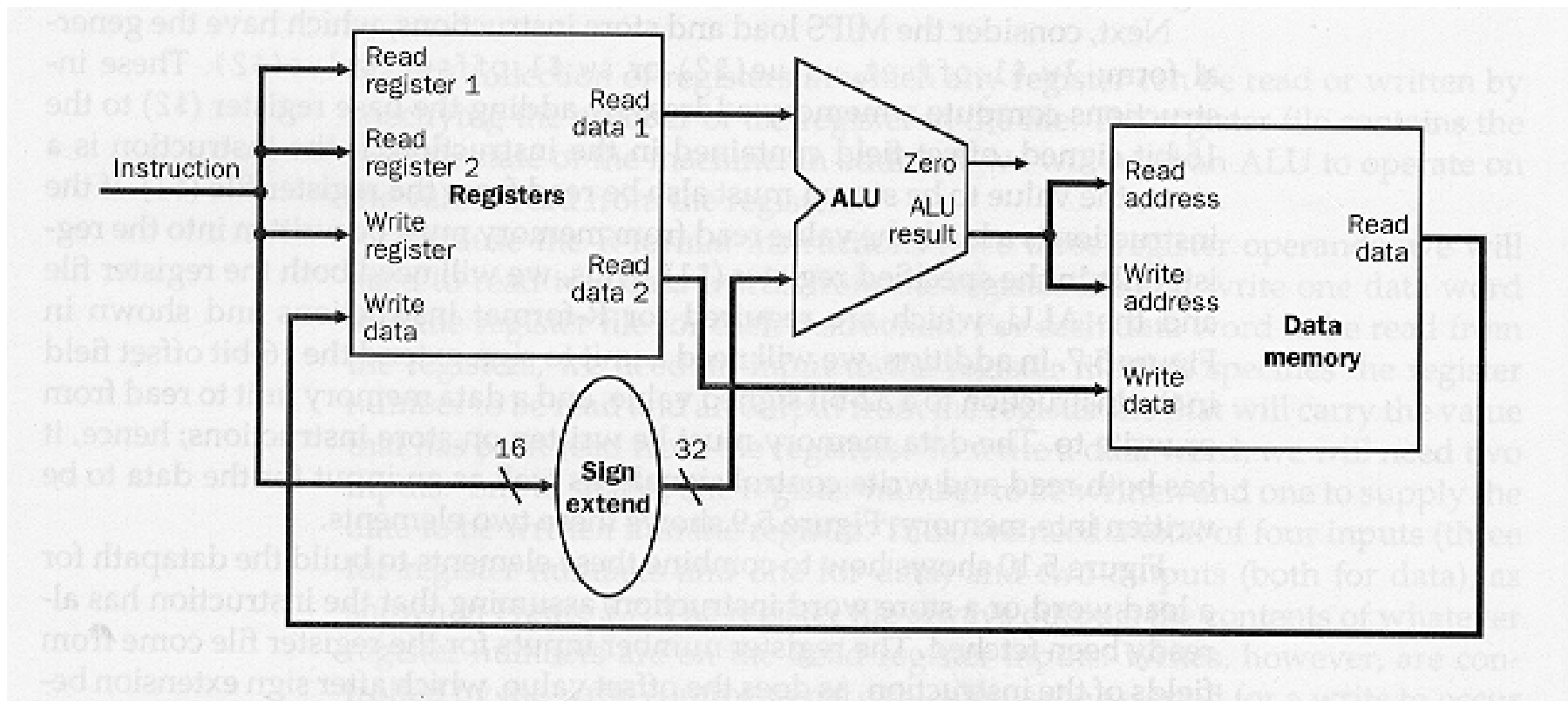

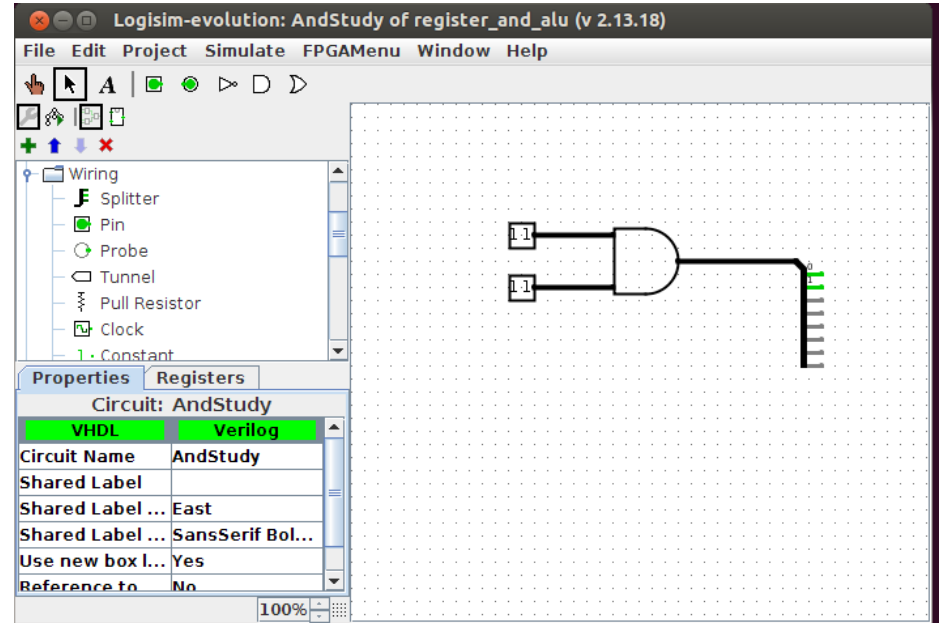- Para implementar a unidade extensão de sinal, podemos usar *splitters*
- A ferramenta Distribuidor (*Splitter*) da biblioteca Base (J) lhe permitirá fazer isso



Memória de Dados



lcad



- Para implementar a memória de dados, usamos a RAM da biblioteca Memory
- Para ativar a escrita, usamos o sinal Write Enable; e a leitura, Output Enable

The screenshot shows the Logisim-evolution interface. On the left, the 'Memory' library is open, showing various components like D Flip-Flop, T Flip-Flop, J-K Flip-Flop, S-R Flip-Flop, Register, Counter, Shift Register, Random Generator, RAM, and ROM. The 'Properties' tab is selected for the 'RAM' component. The 'Registers' tab is also visible. The 'Selection: RAM' table shows the following properties:

VHDL	Verilog
Address Bit Wi...	24
Data Bit Width	32
Trigger	Rising Edge
Databus imple...	One bidirection...
Read write con...	Whole word re...
Contents	(click to edit)
Label	HDL Required
Label Font	SansSerif Bold 16
Label Visible	No

On the right, the RAM component is placed on the circuit board. It is labeled 'RAM 16M x 32'. The internal structure shows a grid of memory cells, with the address bus (A) and data bus (D) connected. The 'Write Enable' (M1) and 'Output Enable' (M2) signals are also shown.


Memória de Dados



lcad



 - Mas note que o componente RAM default possui apenas um barramento para endereço, e apenas um para leitura e escrita
- Assim, mude suas propriedades para que tenha barramentos de leitura e escrita separados (o barramento de endereços é comum à leitura e à escrita)




Memória de Dados



lcad



 - O menor elemento de memória da MIPS ISA é o byte
- Assim, a memória deve permitir o acesso a bytes
- Ela também deve permitir o acesso à half words e words
- Deste modo, ela deve ser composta de quatro unidades de memória de um byte de largura




Memória de Dados



lcad




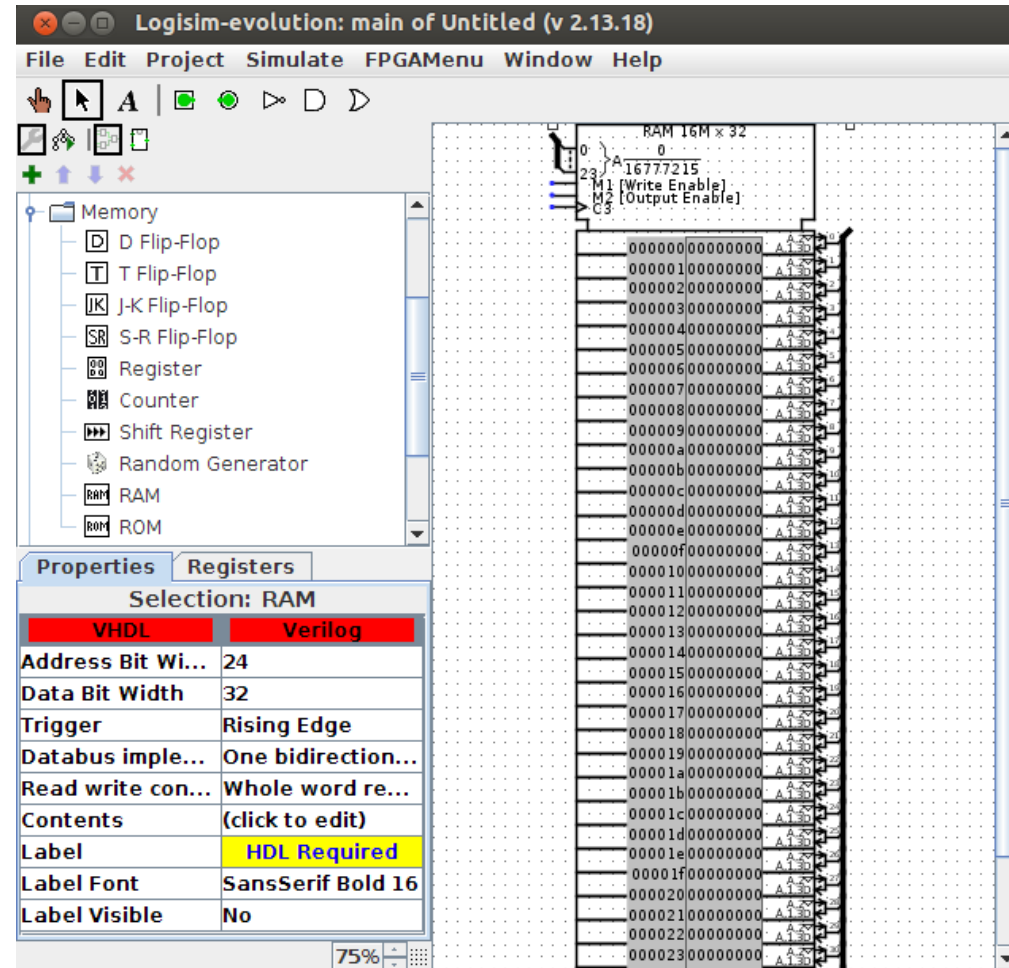- Seu hardware deve permitir acessar para leitura ou escrita:
 - qualquer byte
 - qualquer half word cujo endereço tenha o último bit igual a zero
 - Qualquer word cujo endereço tenha os dois últimos bits iguais a zero
- Use multiplexadores e demultiplexadores para viabilizar estes padrões de acesso





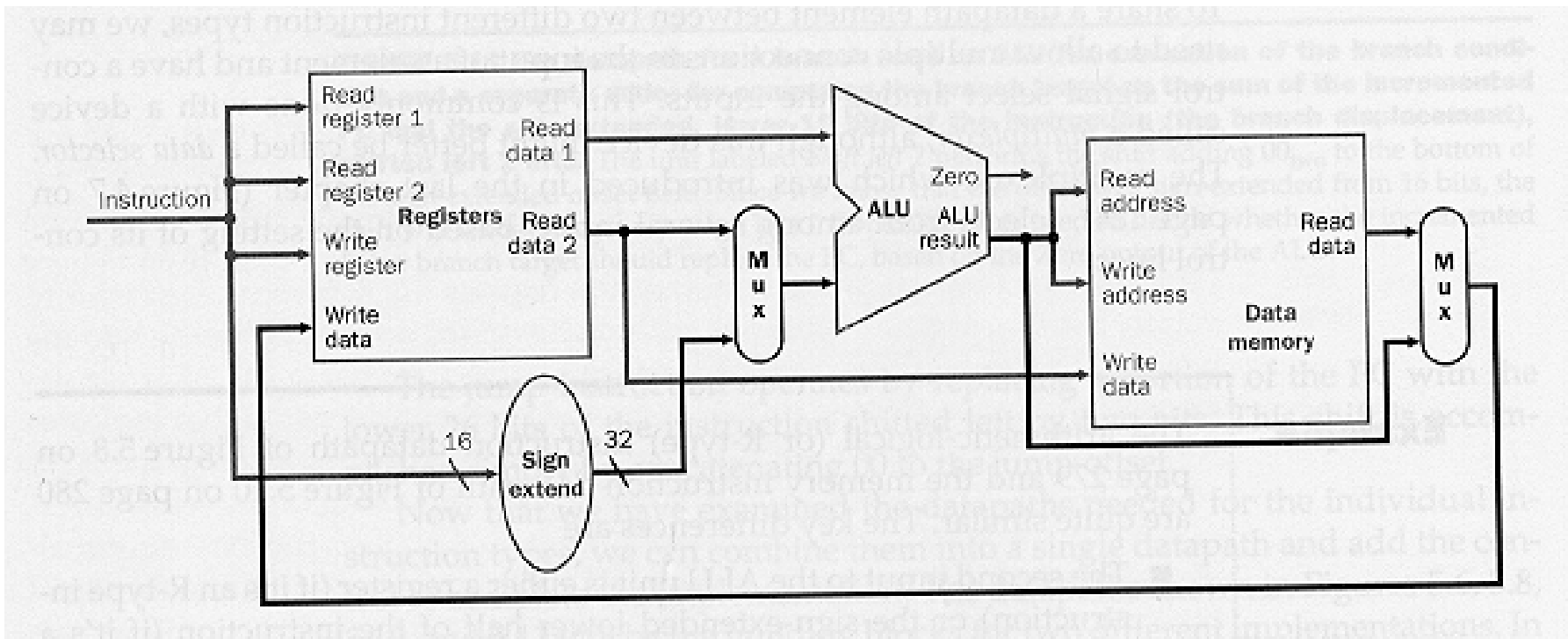- Para juntar o circuito das instruções de acesso à memória ao circuito das instruções aritméticas, podemos empregar multiplexadores




Instruções de Desvio Condicional



lcad



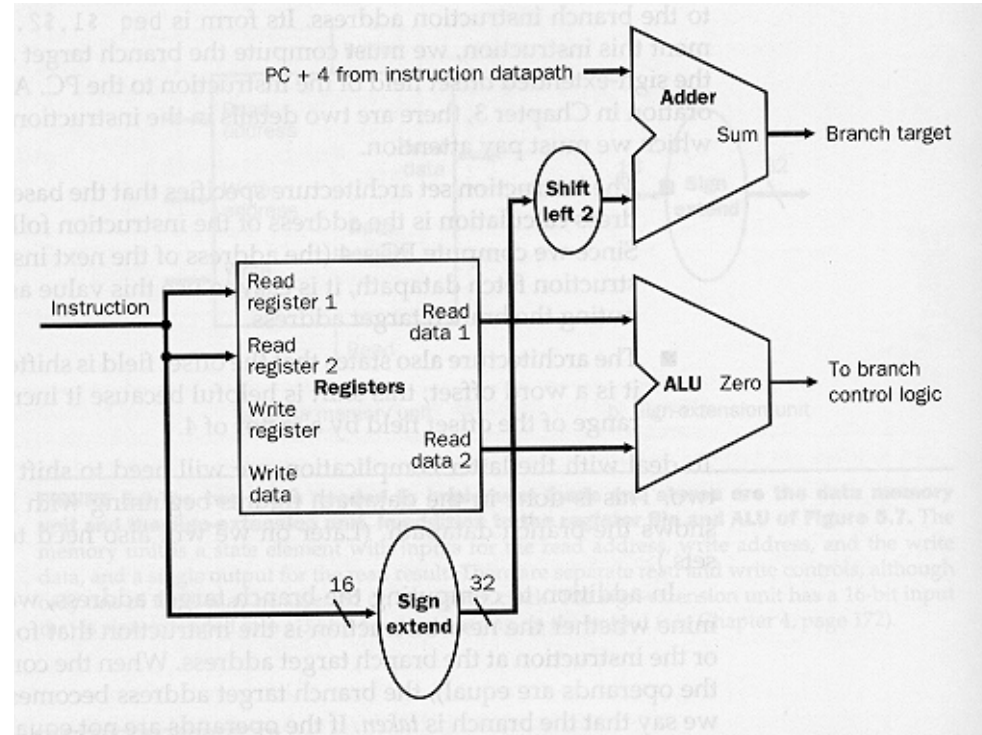- Para implementar as instruções de desvio condicional, podemos usar o circuito ao lado
- A unidade *Shift left 2* pode ser implementada com *splitters* também




Juntando Todos os Circuitos




lcad



- Podemos juntar todos os circuitos que implementamos previamente e vimos hoje como abaixo:

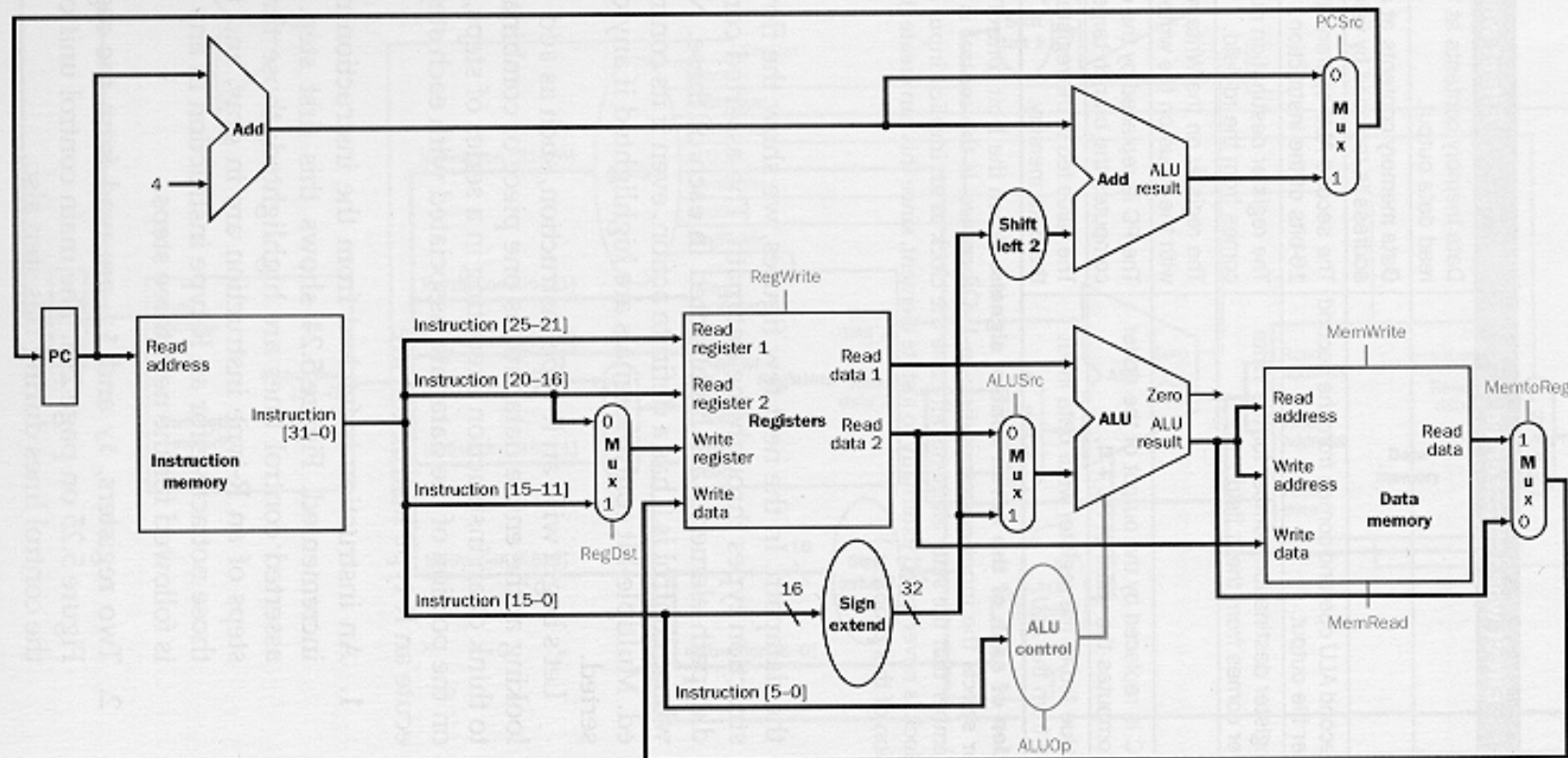


Trabalho 03

 

lcad



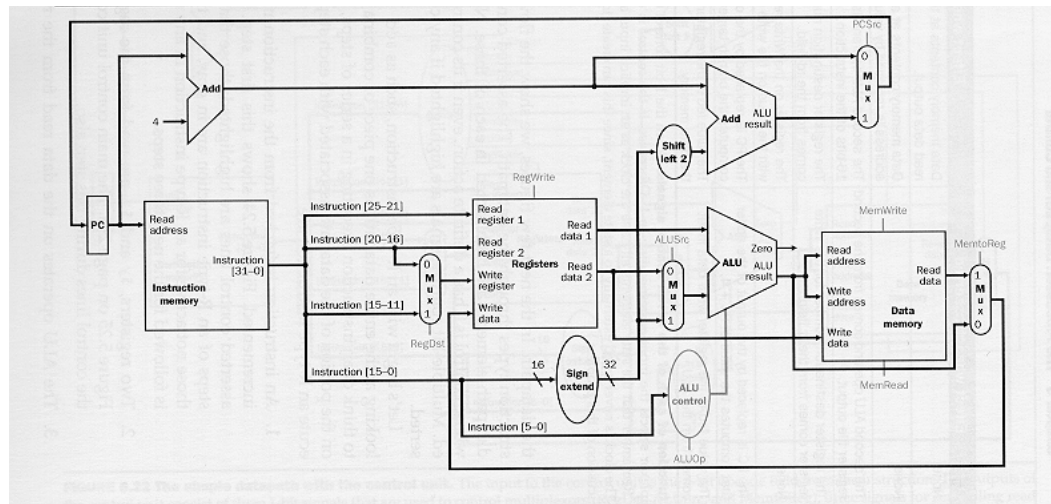- Implemente os circuitos para as instruções de acesso a memória lw, sw, lhu, sh, lbu e sb, e as instruções de desvio condicional beq e bne. Junte estes circuitos aos circuitos implementados previamente como na figura:



- Não é necessário implementar a unidade “ALU control” para o Trabalho 03
- Os trabalhos podem ser feitos em grupos de até 3 alunos e devem ser enviados para sp1@lcad.inf.ufes.br
- **O e-mail deve conter o nome completo dos alunos componentes do grupo**

Category	Instruction	Example	Meaning	Comments
Arithmetic	add	add \$s1,\$s2,\$s3	$\$s1 = \$s2 + \$s3$	Three operands; overflow detected
	subtract	sub \$s1,\$s2,\$s3	$\$s1 = \$s2 - \$s3$	Three operands; overflow detected
	add immediate	addi \$s1,\$s2,100	$\$s1 = \$s2 + 100$	+ constant; overflow detected
	add unsigned	addu \$s1,\$s2,\$s3	$\$s1 = \$s2 + \$s3$	Three operands; overflow undetected
	subtract unsigned	subu \$s1,\$s2,\$s3	$\$s1 = \$s2 - \$s3$	Three operands; overflow undetected
	add immediate unsigned	addiu \$s1,\$s2,100	$\$s1 = \$s2 + 100$	+ constant; overflow undetected
	move from coprocessor register	mfc0 \$s1,\$epc	$\$s1 = \epc	Copy Exception PC + special regs
	multiply	mult \$s2,\$s3	$Hi, Lo = \$s2 \times \$s3$	64-bit signed product in Hi, Lo
	multiply unsigned	multu \$s2,\$s3	$Hi, Lo = \$s2 \times \$s3$	64-bit unsigned product in Hi, Lo
	divide	div \$s2,\$s3	$Lo = \$s2 / \$s3$, $Hi = \$s2 \bmod \$s3$	Lo = quotient, Hi = remainder
Data transfer	divide unsigned	divu \$s2,\$s3	$Lo = \$s2 / \$s3$, $Hi = \$s2 \bmod \$s3$	Unsigned quotient and remainder
	move from Hi	mfhi \$s1	$\$s1 = Hi$	Used to get copy of Hi
	move from Lo	mflo \$s1	$\$s1 = Lo$	Used to get copy of Lo
	load word	lw \$s1,100(\$s2)	$\$s1 = \text{Memory}[\$s2 + 100]$	Word from memory to register
	store word	sw \$s1,100(\$s2)	$\text{Memory}[\$s2 + 100] = \$s1$	Word from register to memory
	load half unsigned	lhu \$s1,100(\$s2)	$\$s1 = \text{Memory}[\$s2 + 100]$	Halfword memory to register
	store half	sh \$s1,100(\$s2)	$\text{Memory}[\$s2 + 100] = \$s1$	Halfword register to memory
	load byte unsigned	lbu \$s1,100(\$s2)	$\$s1 = \text{Memory}[\$s2 + 100]$	Byte from memory to register
Logical	store byte	sb \$s1,100(\$s2)	$\text{Memory}[\$s2 + 100] = \$s1$	Byte from register to memory
	load upper immediate	lui \$s1,100	$\$s1 = 100 * 2^{16}$	Loads constant in upper 16 bits
	and	and \$s1,\$s2,\$s3	$\$s1 = \$s2 \& \$s3$	Three reg. operands; bit-by-bit AND
	or	or \$s1,\$s2,\$s3	$\$s1 = \$s2 \$s3$	Three reg. operands; bit-by-bit OR
	nor	nor \$s1,\$s2,\$s3	$\$s1 = \sim (\$s2 \$s3)$	Three reg. operands; bit-by-bit NOR
	and immediate	andi \$s1,\$s2,100	$\$s1 = \$s2 \& 100$	Bit-by-bit AND with constant
	or immediate	ori \$s1,\$s2,100	$\$s1 = \$s2 100$	Bit-by-bit OR with constant
Conditional branch	shift left logical	sll \$s1,\$s2,10	$\$s1 = \$s2 \ll 10$	Shift left by constant
	shift right logical	srl \$s1,\$s2,10	$\$s1 = \$s2 \gg 10$	Shift right by constant
	branch on equal	beq \$s1,\$s2,25	if ($\$s1 == \$s2$) go to PC + 4 + 100	Equal test; PC-relative branch
	branch on not equal	bne \$s1,\$s2,25	if ($\$s1 != \$s2$) go to PC + 4 + 100	Not equal test; PC-relative
	set on less than	slt \$s1,\$s2,\$s3	if ($\$s2 < \$s3$) $\$s1 = 1$; else $\$s1 = 0$	Compare less than; two's complement
	set less than immediate	slti \$s1,\$s2,100	if ($\$s2 < 100$) $\$s1 = 1$; else $\$s1 = 0$	Compare < constant; two's complement
Unconditional jump	set less than unsigned	sltu \$s1,\$s2,\$s3	if ($\$s2 < \$s3$) $\$s1 = 1$; else $\$s1 = 0$	Compare less than; natural numbers
	set less than immediate unsigned	sltiu \$s1,\$s2,100	if ($\$s2 < 100$) $\$s1 = 1$; else $\$s1 = 0$	Compare < constant; natural numbers
	jump	j 2500	go to 10000	Jump to target address
	jump register	jr \$ra	go to \$ra	For switch, procedure return
	jump and link	jal 2500	$\$ra = PC + 4$; go to 10000	For procedure call



lcad

